

NETWORK ANALYSIS AND SYNTHESIS

(UE21EC242A)

PROJECT

TEAM MEMBERS

ANKUR PANDEY(PES1UG21EC048)

TEJAS V P(PES1UG21EC910)

AKASH BHAT(PES1UG21EC025)

SALLEN KEY BAND
PASS FILTER

CONTENTS:

- 1-> INTRODUCTION**
- 2->EXPLANATION**
- 3->ADVANTAGES**
- 4->CIRCUITS**
- 5->SIMULATION**
- 6->CALCULATIONS**
- 7->APPLICATIONS**

Sallen-Key is one of the most common filter configurations for designing first-order (1st-order) and second-order (2nd-order) filters and as such is used as the basic building blocks for creating much higher order filters.

EXPLANATION:

We have seen here in this tutorial that the Sallen-Key configuration, also known as a voltage-controlled, voltage-source (VCVS) circuit is the most widely used filter topologies due mainly to the fact that the operational amplifier used within its design can be configured as a unity gain buffer or as a non-inverting amplifier.

The basic Sallen-key filter configuration can be used to implement different filter responses such as, Butterworth, Chebyshev, or Bessel with the correct selection of RC filter network. Most practical values of R and C can be used remembering that for a specific cut-off frequency point, the values of R and C are inversely proportional. That is as the value of R is made smaller, C becomes larger, and vice versa.


The Sallen-key is a 2nd-order filter design which can be cascaded together with other RC stages to create higher-order filters. Multiple filter stages need not be the same but can each have different cut-off frequency or gain characteristics. For instance, putting together a low-pass stage and a high-pass stage to create a Sallen and Key band-pass filter.

Here we have looked at designing a Sallen-key high-pass filter, but the same rules apply equally for a Sallen-key low-pass design. The voltage gain, AV of the op-amp determines its response. The voltage gain is preset by the two voltage divider resistors, R_1 and R_2 remembering that the voltage gain must always be less than 3 otherwise, the filter circuit will become unstable and oscillate.

ADVANTAGES:


- Simple design
- Voltage gain control
- Cascading of filters
- Attenuator to an amplifier
- Wide frequency range
- Different configurations
- Multiple stages and different gains
- Stability

CIRCUIT

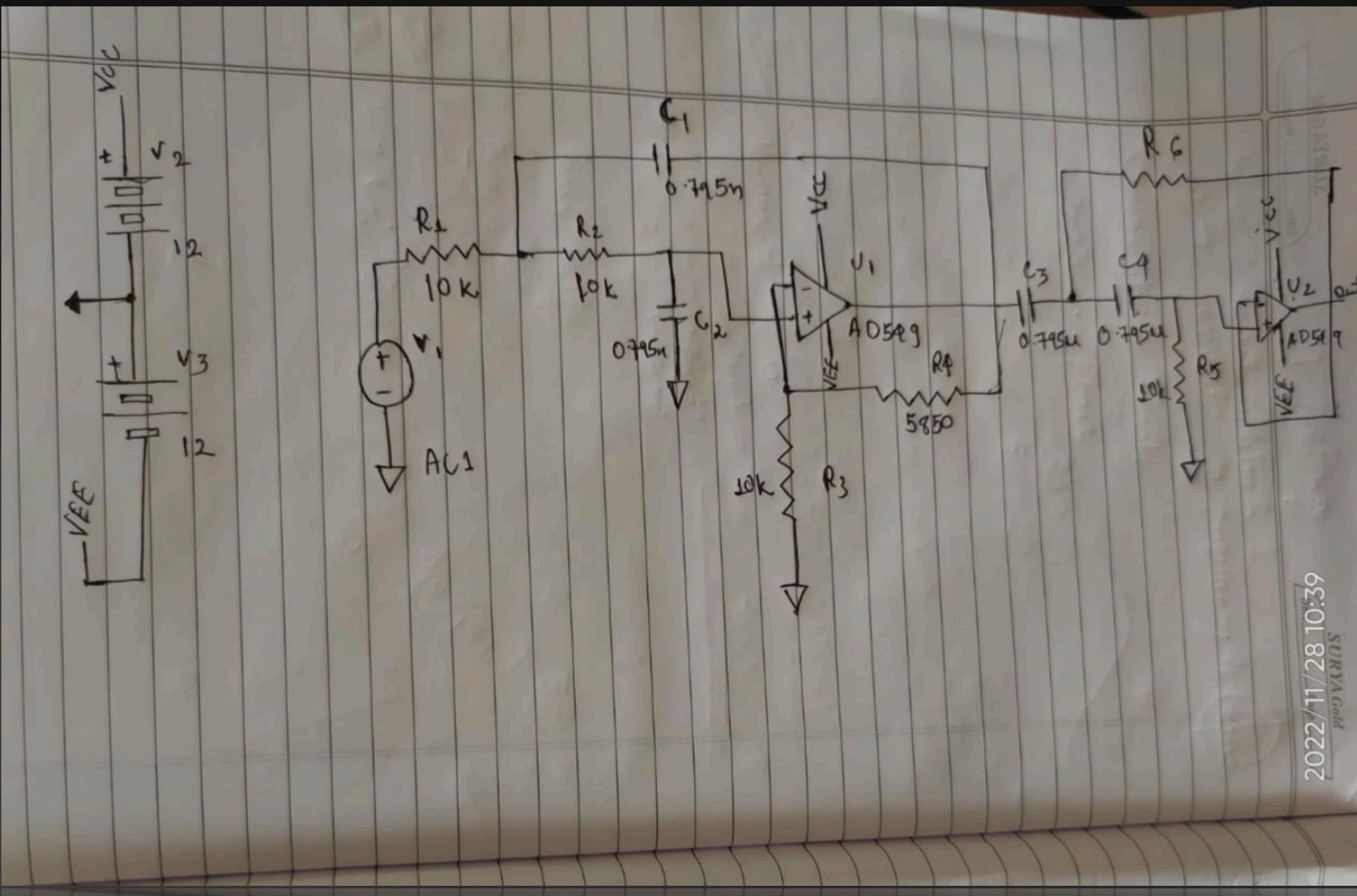

28/11/2022

SIMULATIONS:

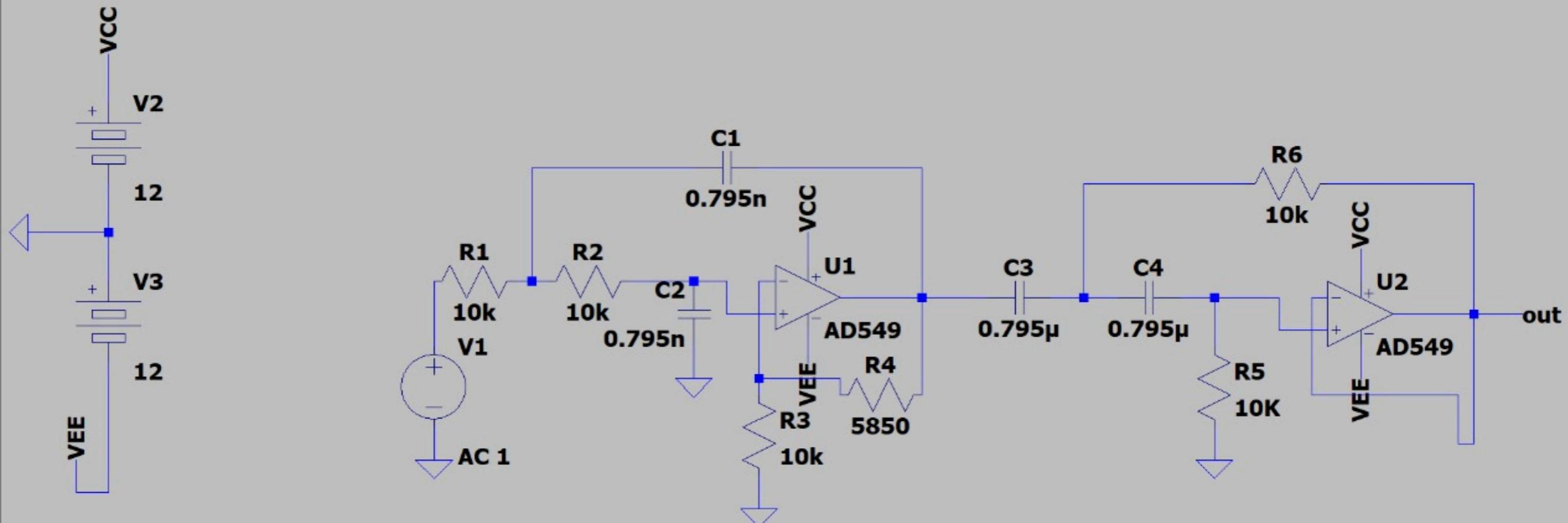


.ac lin 100 3 30K


OUTPUT- >




AT 20KHZ

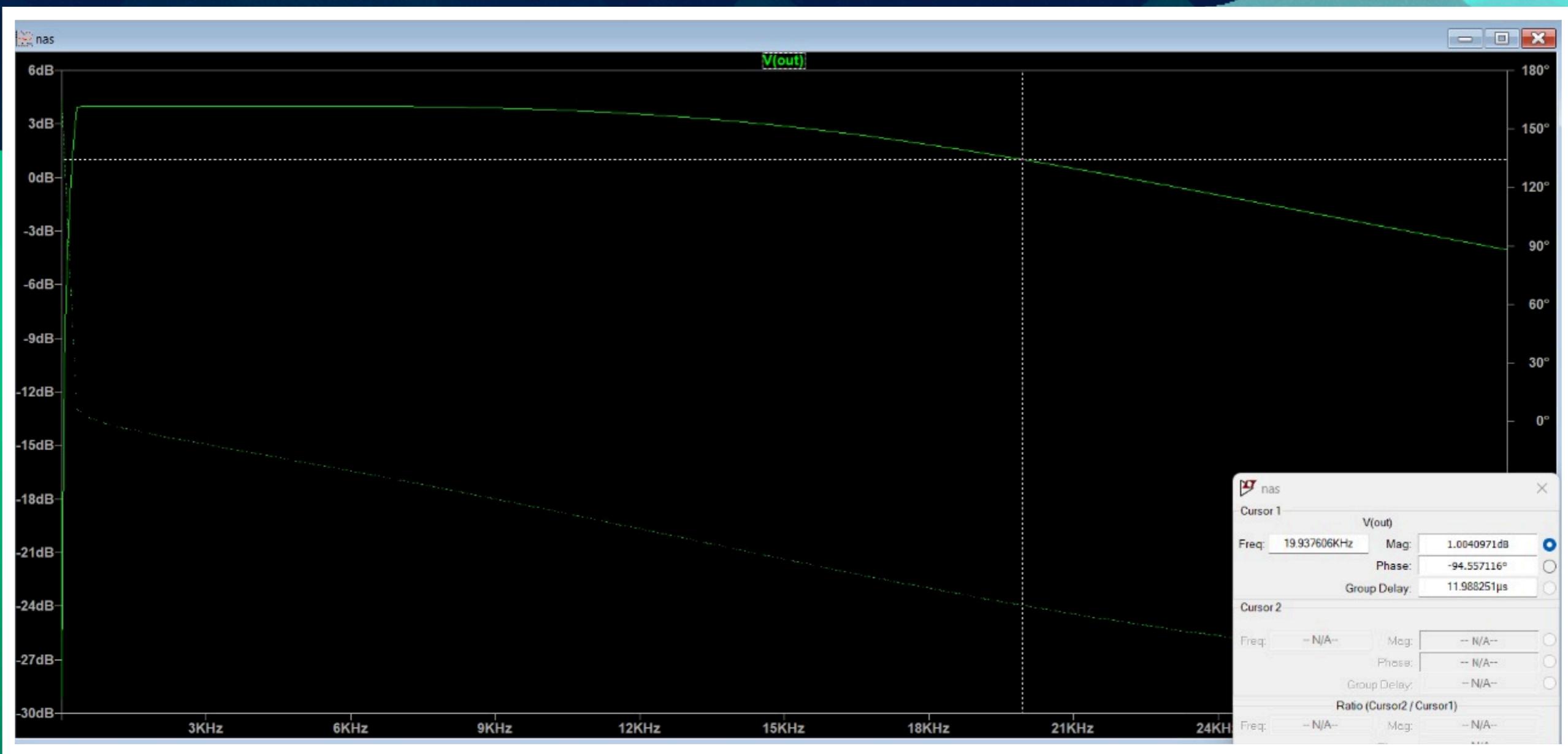

AT 20 HZ

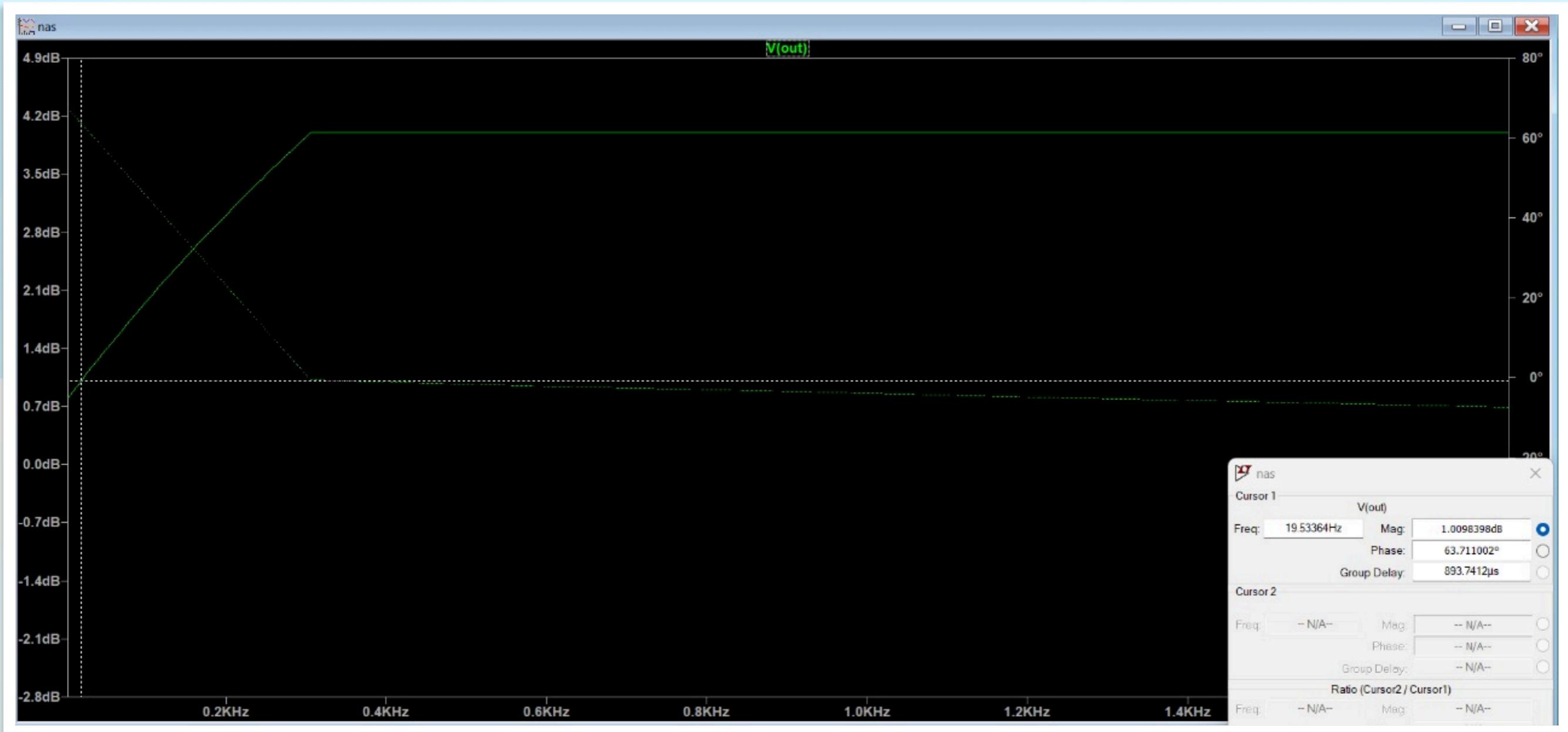

ABOVE 20 KHZ

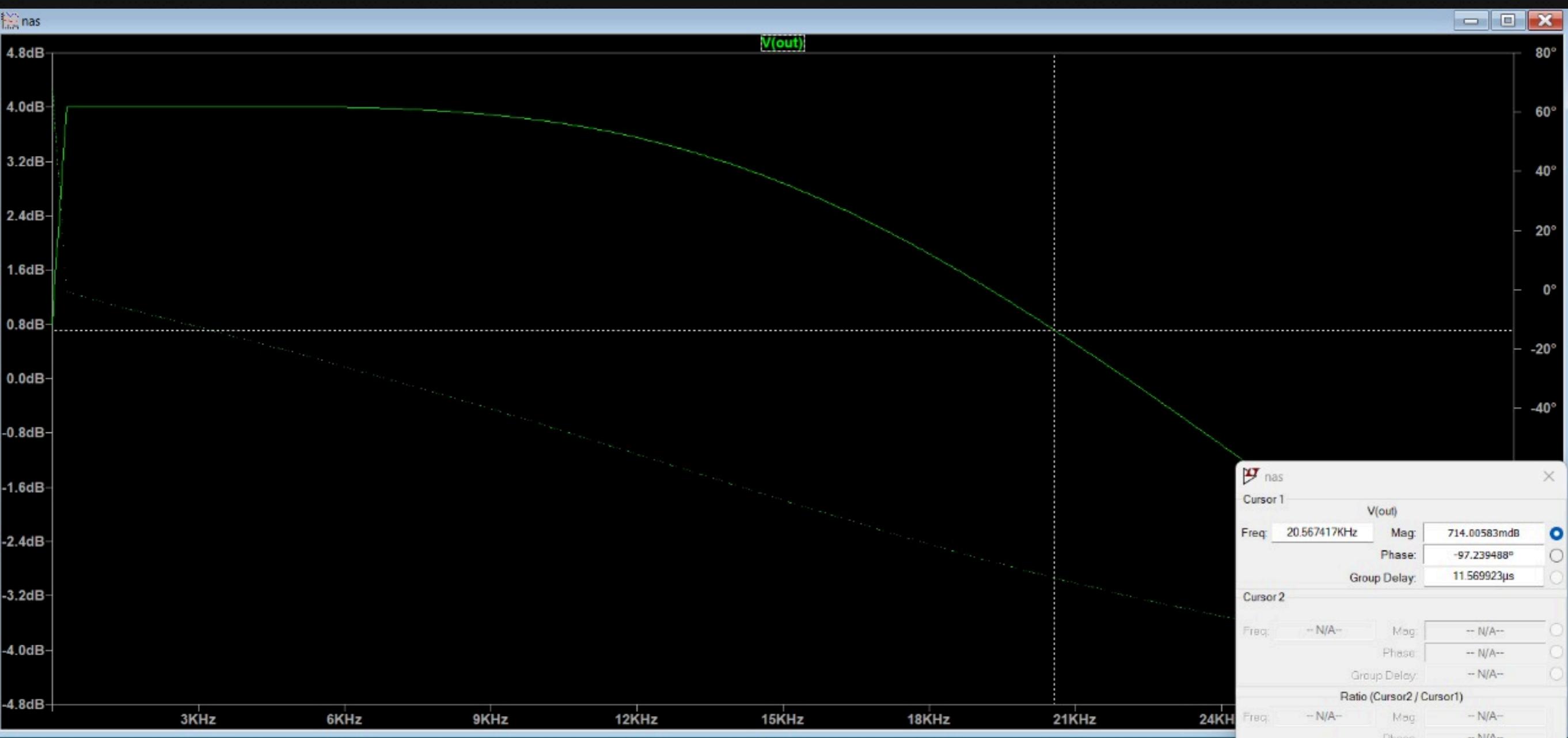

CALCULATIONS:

ABSOLUTE MAXIMUM RATINGS

Table 2.

Parameter	Rating
Supply Voltage	$\pm 18\text{ V}$
Internal Power Dissipation	500 mW
Input Voltage ¹	$\pm 18\text{ V}$
Output Short-Circuit Duration	Indefinite
Differential Input Voltage	$+V_S$ and $-V_S$
Storage Temperature Range	-65°C to +125°C
Operating Temperature Range AD549J, AD549K, AD549L AD549S	0°C to +70°C -55°C to +125°C
Lead Temperature (Soldering, 60 sec)	300°C

¹ For supply voltages less than $\pm 18\text{ V}$, the absolute maximum input voltage is equal to the supply voltage.

$$f_c = \frac{1}{2\pi RC}$$

$$Q = \frac{1}{3-K}$$

$Q = \frac{1}{\sqrt{2}}$ we will take general Q factor to consideration

$$3-K = \sqrt{2}$$

$$K = 3 - \sqrt{2}$$

$$K = 1.585$$

$$K = 1 + \frac{R_4}{R_3}$$

$$\frac{R_4}{R_3} = 0.585$$

Let assume $R_3 = 10k$

$$R_4 = 5850 \text{ ohms}$$

Audi

Audible frequency

20 Hz to 20 kHz

$$F_c = 20 \text{ kHz}$$

$$F_c = \frac{1}{2\pi R C}$$

Let $R = 10k$

$$C = \frac{1}{2\pi R F_c}$$

$$C = \frac{1}{2\pi * 20k * 10k}$$

$$C = 0.795 \text{ nF}$$

Applications:

The applications include:

They are widely used in wireless transmitters and receivers in signal processing. The main function of this filter is to restrict the bandwidth of the o/p signal that is allocated for transmission.

It evades the transmitter from meddling with other stations.

It decodes signals from a particular range of frequencies while stopping signals from unwanted frequencies to pass through. It also enhances the signal to noise ratio and sensitivity in a receiver environment.

They are deployed in all kinds of electronic and communication devices, biomedical devices like EEG's, electrocardiograms, seismology etc.

It is popularly used in optical field too, like Lasers, LIDARs, etc.

It is used in finding meteorological data to understand the weather forecasts during a particular range of time. For example, finding out weather report of specific area from a time range of 3-10 days time period.

THANK YOU->